

Experiment #2 - FPGA Realization of Radix-4 Multiplier

Ava Mir - Nesa Abbasi,
810199501- 810199457

1.1

 


Fig. 1 DataPath

1.2

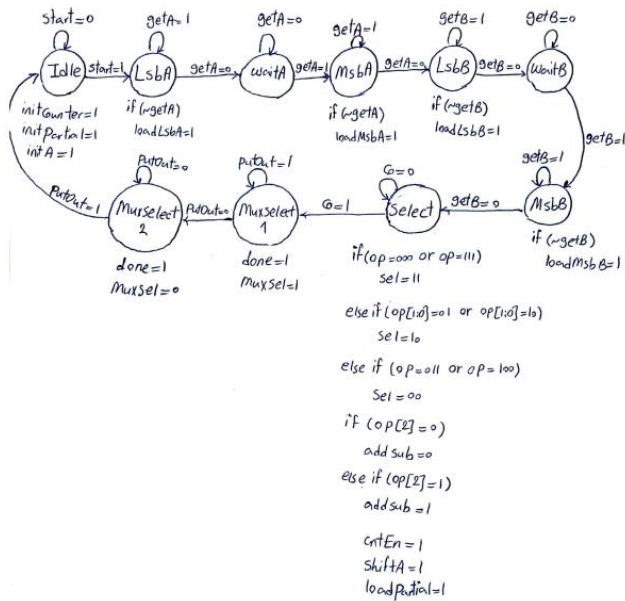


Fig. 2 Controller

1.3

```
module DataPath(output [15:0] out, output [2:0] selA, input loadLsbA, loadMsbA, loadLsbB, loadMsbB, initA,
initP, shiftA, loadPartial, input [7:0] in, input [1:0] selMux, input selAddSub, muxSel, clk, rst);
    wire [16:0] outA;
    wire [15:0] outB, shiftB, outP, outMux, addSubOut;
    assign shiftB = outB << 2;
    wire [31:0] Res;
    assign Res = {addSubOut, outA[16:1]};
    assign selA = outA[2:0];
    ShiftRegA registerSHA(outA, clk, rst, initA, loadLsbA, loadMsbA, shiftA, addSubOut[1:0], in);
    RegB registerB(outB, clk, rst, loadLsbB, loadMsbB, in);
    RegPartial registerP(outP, clk, rst, initP, loadPartial, {addSubOut[15], addSubOut[15:2]});
    MUX mux(outMux, selMux, shiftB, 16'd0, outB, 16'd0);
    Adder addSub(addSubOut, selAddSub, outMux, outP);
    Mux2 mux2(out, muxSel, Res);
endmodule
```

Fig. 3 DataPath Verilog

```
module controller(output reg selAddSub, initPartial, initA, loadLsbA, loadLsbB, loadMsbA, loadMsbB, loadPartial,
shiftA, muxSel, done, output reg [1:0] sel, input getA, getB, start, putOut, clk, rst,
input [2:0] opc);
    wire co;
    reg cntEn, initCounter;
    reg [2:0] counter;
    reg [3:0] ns,ps;
    parameter [3:0] Idle = 0, LsbA = 1, WaitA = 2, MsbA = 3, LsbB=4, WaitB =5, MsbB=6, Select = 7, MuxSelect1 = 8,
MuxSelect2 = 9;
    always@(ps, opc, co, getA, getB, start, putOut)begin
        ns = Idle;
        {initCounter, initPartial, initA, shiftA, loadLsbA, loadMsbA, loadLsbB, loadMsbB, cntEn, loadPartial,
selAddSub, muxSel, done} = 13'd0;
        case(ps)
            Idle: begin
                ns = start ? LsbA : Idle;
                {initCounter, initPartial, initA} = 3'b111;
            end
            LsbA: begin
                ns = getA ? LsbA : WaitA;
                loadLsbA = getA ? 1'b0 : 1'b1;
            end
            WaitA: begin
                ns = getA ? MsbA : WaitA;
            end
            MsbA: begin
                ns = getA ? MsbA : LsbB;
                loadMsbA = getA ? 1'b0 : 1'b1;
            end
            LsbB: begin
                ns = getB ? LsbB : WaitB;
                loadLsbB = getB ? 1'b0 : 1'b1;
            end
            WaitB: begin
                ns = getB ? MsbB : WaitB;
            end
            MsbB: begin
                ns = getB ? MsbB : Select;
                loadMsbB = getB ? 1'b0 : 1'b1;
            end
            Select: begin
                ns = co ? MuxSelect1 : Select;
                {cntEn, shiftA, loadPartial} = 3'b111;
                if(opc == 3'b000)
                    sel = 2'b11;
                else if(opc == 3'b111)
                    sel = 2'b11;
                else if(opc == 3'b011)
                    sel = 2'b00;
                else if(opc == 3'b100)
                    sel = 2'b00;
                else if(opc[1:0] == 2'b01)
                    sel = 2'b10;
                else if(opc[1:0] == 2'b10)
                    sel = 2'b10;
                if(opc[2] == 0)
                    selAddSub = 1'b0;
                else if(opc[2] == 1)
                    selAddSub = 1'b1;
            end
            MuxSelect1: begin
                ns = putOut ? MuxSelect1 : MuxSelect2;
                muxSel = 1'b1;
                done = 1'b1;
            end
            MuxSelect2: begin
                ns = ~putOut ? MuxSelect2 : Idle;
                muxSel = 1'b0;
                done = 1'b1;
            end
        endcase
    end
    always@(posedge clk, posedge rst)begin
        if(rst)
            ps <= Idle;
        else
            ps <= ns;
        end
    always @(posedge clk, posedge rst) begin
        if (rst)
            counter <= 3'd0;
        else if(cntEn)
            counter <= counter + 1'b1;
        else if(initCounter)
            counter <= 3'd0;
    end
    assign co = &counter;
endmodule
```

Fig. 4 Controller Verilog

1.4

```
timescale 1ns/1ns
module TestBench();
  wire [15:0] Res;
  wire [6:0] HEX0, HEX1, HEX2, HEX3;
  wire done;
  reg [7:0] in ;
  reg clk = 1'b1;
  reg rst;
  reg putOut;
  reg getA = 1'b1;
  reg getB = 1'b1;
  reg start = 1'b0;
  Radix4Multiplier radix4(Res, HEX0, HEX1, HEX2, HEX3, done, in, start, getA, getB, putOut, clk, rst);
  always #10 clk = ~clk;
  initial begin
    #17 rst = 1'b1;
    #17 rst = 1'b0;
    #17 start = 1'b1;
    in = 8'd3;
    #26 getA = 1'b0;
    #23 in = 8'd0;
    #56 getA = 1'b1;
    #56 getA = 1'b0;
    #30 in = 8'd5;
    #26 getB = 1'b0;
    #30 in = 8'd0;
    #26 getB = 1'b1;
    #26 getB = 1'b0;
    #150 putOut = 1'b1;
    #30 putOut = 1'b0;
    #2000 $stop;
  end
endmodule
```

Fig. 5 TestBench Verilog

1.5

We enter 3 for A input and 5 for B input. First we enter 8'd0 for MsbA and 8'd3 for LsbA, then we enter 8'd0 for MsbB and 8'd5 for LsbB. 8'd15 will be received as Lsb of the output and 8'd0 will be received as Msb of the output. The end result is what we expected.

 


Fig. 6 Waveform

2.5

 


Fig. 7 RTL View

2.7

We pressed buttons in following orders:

1. Rst
2. Press Start button(Key2)
3. Show 8'd0 with switches
4. Press GetA button(Key0)
5. Show 8'd3 with switches
6. Press GetA button(Key0)
7. Show 8'd0 with switches
8. Press GetB button(Key1)
9. Show 8'd5 with switches
10. Press GetB button(Key1)
11. Press PutOut button(Key3)
12. Press PutOut button(Key3)

After we pressed the PutOut button for the first time, We received the Lsb of the output which is 4'hF(15 in Decimal). And when we pressed the PutOut button for the second time, We received the Msb of the output which is 4'h0(0 in Decimal). So the final output was 15 as we expected.

 


Fig. 8 FPGA Result(Lsb)

 


Fig. 9 FPGA Result(Msb)