

# Experiment #4 – Accelerator and Wrappers

Ava Mirmohammadmahdi 810199501  
Nesa Abbasi 810199457

## 1. Exponential Engine

### 1.1

```
timescale 1ns/1ns

module ExpTest0;
  wire [15:0] fractionalPart;
  wire [110] integerPart;
  wire done;

  reg [15:0] x;
  reg clk = 1'b0, rst = 1'b0, start = 1'b0;

  exponential Exp(x(x), .start(start), .clk(clk), .rst(rst), .done(done), .intpart(integerPart), .fracpart(fractionalPart));

  always #5 clk = ~clk;

  initial begin
    #1 rst = 1'b1;
    #1 rst = 1'b0;
    #10 x = 16'h0000;
    #0 start = 1'b1;
    #10 start = 1'b0;
    while (~done) #10;
    #100;
    #10 x = 16'hCCCC;
    #0 start = 1'b1;
    #10 start = 1'b0;
    while (~done) #10;
    #100;
    #10 x = 16'h3333;
    #0 start = 1'b1;
    #10 start = 1'b0;
    while (~done) #10;
    #100;
    #10 x = 16'hFD70;
    #0 start = 1'b1;
    #10 start = 1'b0;
    while (~done) #10;
    #100;
    #10 x = 16'h028F;
    #0 start = 1'b1;
    #10 start = 1'b0;
    while (~done) #10;
    #100;
    #100 $stop;
  end
endmodule
```

Fig. 1 Verilog Testbench

 


Fig. 2 Simulation

Input 0x8000 → 0x0A5E3

Input 0xCCC → 0x233F7

Input 0x3333 → 0x13581

Input 0xFD70 → 0x2B01E5

Input 0x028F → 0x10000

The difference is because of the exponential engine.

### 1.2

| Flow Summary                       |  |
|------------------------------------|--|
| Flow Status                        | Successful - Tue May 17 05:52:58 2022    |
| Quartus II 64-Bit Version          | 12.1 Build 177 11/07/2012 SJ Web Edition |
| Revision Name                      | ExpAcc                                   |
| Top-level Entity Name              | ExpEngine                                |
| Family                             | Cyclone II                               |
| Device                             | EP2C20F484C7                             |
| Timing Models                      | Final                                    |
| Total logic elements               | 102 / 18,752 ( < 1 % )                   |
| Total combinational functions      | 100 / 18,752 ( < 1 % )                   |
| Dedicated logic registers          | 61 / 18,752 ( < 1 % )                    |
| Total registers                    | 61                                       |
| Total pins                         | 38 / 315 ( 12 % )                        |
| Total virtual pins                 | 0  |
| Total memory bits                  | 0 / 239,616 ( 0 % )                      |
| Embedded Multiplier 9-bit elements | 2 / 52 ( 4 % )                           |
| Total PLLs                         | 0 / 4 ( 0 % )                            |

Fig. 3 Synthesis result

### 1.3

| Slow Model Fmax Summary |                 |            |      |
|-------------------------|-----------------|------------|------|
| Fmax                    | Restricted Fmax | Clock Name | Note |
| 113.22 MHz              | 113.22 MHz      | clk        |      |

Fig. 4 Maximum frequency

## 2. The Wrapper Controller

### 2.1

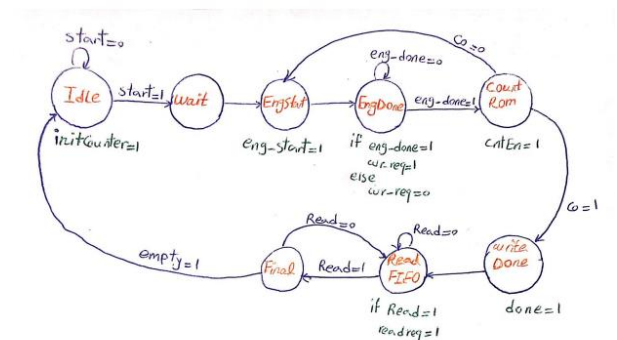


Fig. 5 State Diagram

```

module ControllerAcc(input clk, rst, start, read, eng_done, empty, output reg eng_start, writeReq, done, readReq,
output reg[2:0] counter);
    reg [2:0] ps, ns;
    reg cntEn, initCounter;
    wire co;
    parameter [2:0] Idle = 0, Wait = 1, EngStart = 2, EngDone = 3, CountRom = 4, WriteDone = 5, ReadFIFO = 6,
    Final = 7;
    always @(ps, start, eng_done, co, read, empty) begin
        ns = Idle;
        {initCounter, cntEn, writeReq, eng_start, done, readReq} = 7'd0;
        case (ps)
            Idle: begin
                ns = start ? Wait : Idle;
                initCounter = 1'b1;
            end
            Wait: begin
                ns = EngStart;
            end
            EngStart: begin
                ns = EngDone;
                eng_start = 1'b1;
            end
            EngDone: begin
                ns = eng_done ? CountRom : EngDone;
                writeReq = eng_done ? 1'b1 : 1'b0;
            end
            CountRom: begin
                ns = co ? WriteDone : EngStart;
                cntEn = 1'b1;
            end
            WriteDone: begin
                ns = ReadFIFO;
                done = 1'b1;
            end
            ReadFIFO: begin
                ns = read ? Final : ReadFIFO;
                readReq = read ? 1'b1 : 1'b0;
            end
            done = 1'b1;
            end
            Final: begin
                ns = empty ? Idle : ~read ? ReadFIFO : Final;
                done = 1'b1;
            end
            endcase
        end

    always @(posedge clk, posedge rst) begin
        if (rst)
            ps <= Idle;
        else
            ps <= ns;
        end

    always @(posedge clk, posedge rst) begin
        if (rst)
            counter <= 3'd0;
        else if (initCounter)
            counter <= 3'd0;
        else if (cntEn)
            counter <= counter + 1'b1;
        end
        assign co = &counter;
    end
endmodule

```

Fig. 6 Controller Verilog

2.2

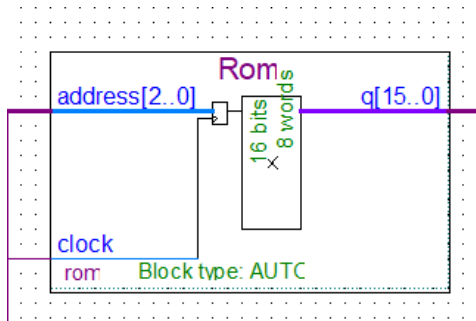


Fig. 7 Rom IP

```

WIDTH=16;
DEPTH=8;
ADDRESS_RADIX=HEX;
DATA_RADIX=HEX;
CONTENT BEGIN
00 : 8000;
01 : CCCC;
02 : 3333;
03 : FD70;
04 : 028F;
05 : 0000;
06 : 0000;
07 : 0000;
END;

```

Fig. 8 Mif File

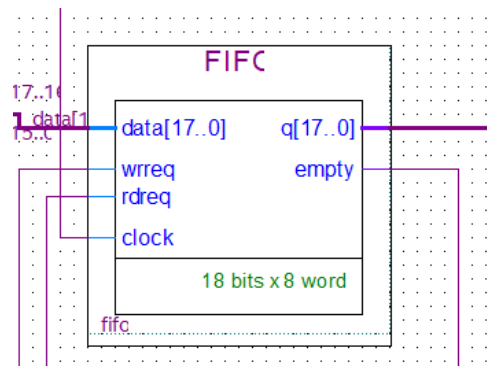


Fig. 9 FIFO IP

 


Fig. 10 The accelerator block diagram

2.4

```

module AcceleratorTB();
    reg start, read, clk, rst;
    wire done;
    wire [17:0] out;

    Accelerator acc(.done(done), .start(start), .clk(clk), .rst(rst), .read(read), .out(out));

    always #5 clk = ~clk;

    initial begin
        #0 clk = 0; rst = 0; start = 0; read = 0;
        #3 rst = 1;
        #3 rst = 0;
        #10 start = 1;
        while (~done) #10;
        #30 read = 1;
        #30 read = 0;
        #30 read = 1;
        #30 read = 0;
        #30 read = 1;
        #30 read = 0;
        #30 read = 1;
        #30 read = 0;
        #30 read = 1;
        #30 read = 0;
        #30 read = 1;
        #30 read = 0;
        #30 read = 1;
        #30 read = 0;
        #30 read = 1;
        #30 read = 0;
        #30 read = 1;
        #30 read = 0;
        #100 $stop;
    end
endmodule

```

Fig. 11 Accelerator Testbench

2.5

 


Fig. 12 Complete pulse on signal "start"

2.6

 


Fig. 13 Simulation result

### 3.Implementing Accelerator on FPGA

#### 3.1

| Flow Summary                       |   |
|------------------------------------|---|
| Flow Status                        | Successful - Sat Jun 18 20:19:05 2022       |
| Quartus Prime Version              | 20.1.0 Build 711 06/05/2020 SJ Lite Edition |
| Revision Name                      | Accelerator                                 |
| Top-level Entity Name              | Accelerator                                 |
| Family                             | Cyclone IV E                                |
| Total logic elements               | 135 / 6,272 ( 2 % )                         |
| Total registers                    | 83  |
| Total pins                         | 23 / 92 ( 25 % )                            |
| Total virtual pins                 | 0   |
| Total memory bits                  | 272 / 276,480 ( < 1 % )                     |
| Embedded Multiplier 9-bit elements | 2 / 30 ( 7 % )                              |
| Total PLLs                         | 0 / 2 ( 0 % )                               |
| Device                             | EP4CE6E22C6                                 |
| Timing Models                      | Final                                       |

Fig. 14 Synthesis report

#### 3.2

We connected Done signal to LED 9, Start pin to SW9 and Read to SW0. We read the results one by one by setting SW0 to one. After LED9 turned on.

#### 3.3

```
module Final(input [15:0] in, output [6:0] HEX0, HEX1, HEX2, HEX3);
  Hexdisplay HD1 (in[3:0], HEX0);
  Hexdisplay HD2 (in[7:4], HEX1);
  Hexdisplay HD3 (in[11:8], HEX2);
  Hexdisplay HD4 (in[15:12], HEX3);
endmodule
```

Fig. 15 Converter for 7 Segment display

To convert data for 7 segment display, we omitted 2 least significant bits.

#### 3.4

 


Fig. 16 First output

18 bits binary → Omit 2 least significant bits → Hex  
011010011000001011 → 011010011000001011 → 6982



Fig. 17 Second output

18 bits binary → Omit 2 least significant bits → Hex  
100011100110110011 → 100011100110110011 → 8E6C



Fig. 18 Third output

18 bits binary → Omit 2 least significant bits → Hex  
010011100010101000 → 010011100010101000 → 4E2A

 


Fig. 19 Fourth output

18 bits binary → Omit 2 least significant bits → Hex  
101011000011101001 → 101011000011101001 → AC3A





Fig. 20 Fifth output

18 bits binary  $\rightarrow$  Omit 2 least significant bits  $\rightarrow$  Hex  
 $010000001010001111 \rightarrow 010000001010001144 \rightarrow 40A3$



Fig. 21 Sixth output

18 bits binary  $\rightarrow$  Omit 2 least significant bits  $\rightarrow$  Hex  
 $001111111111111111 \rightarrow 001111111111111144 \rightarrow 3FFF$

If we convert our 18 bit input from hex to binary and ommit 2 least significant bits of it and then convert it to hex the output is the same as we epected.