

Experiment #3– Function Generator

Ava Mirmohammadmahdi 810199501
Nesa Abbasi 810199457

1.Digital to Analog conversion using PWM

1.1

```
module DAC(output reg out,input[7:0]in,input clk,rst);
    reg[7:0] counter;
    always @(posedge clk, negedge rst) begin
        if(~rst)
            counter <= 8'd0;
        else
            counter <= counter + 1'b1;
    end
    always@(counter,in)begin
        if(counter > in)
            out = 1'b0;
        else
            out = 1'b1;
    end
endmodule
```

Fig. 1 Dac verilog

1.2



Fig. 2 Dac waveform

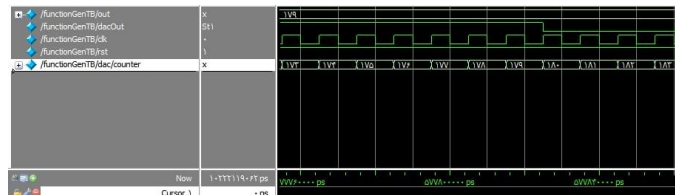


Fig. 3 Dac waveform

As we see when input < counter, the output is 0 else is 1.

2.Waveform Generator

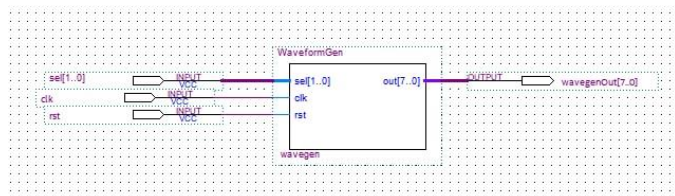


Fig. 4 Waveform generator

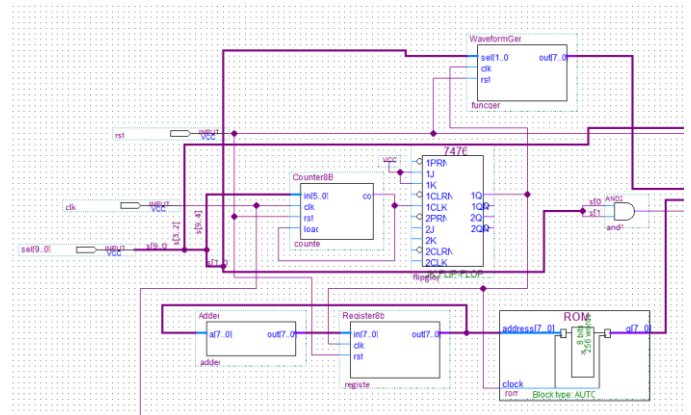


Fig. 5 Waveform generator

1.

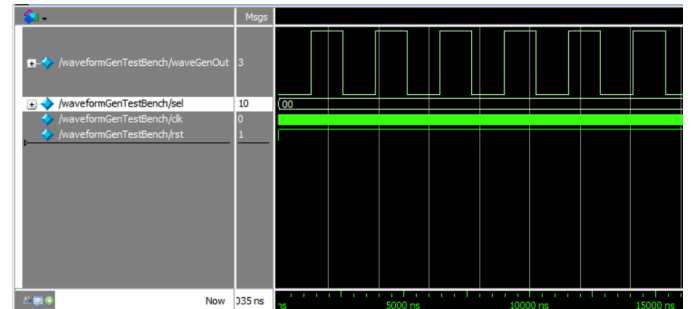


Fig. 6 Square output

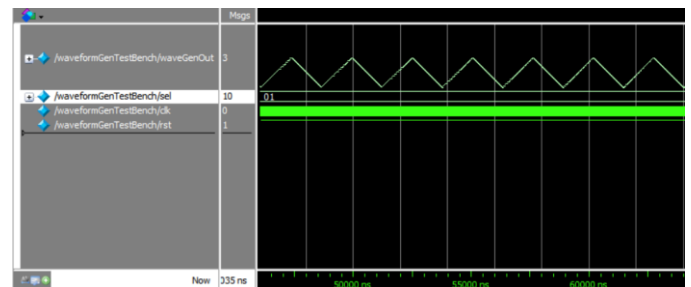


Fig. 7 Triangle output

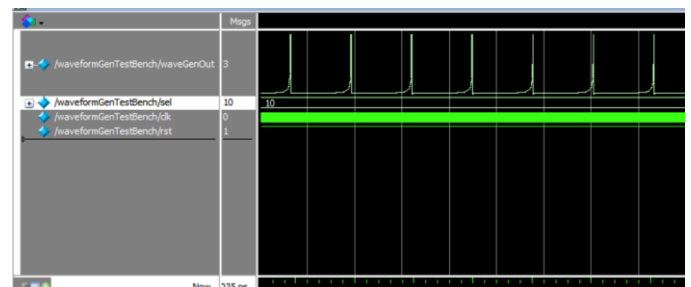


Fig. 8 Reciprocal output

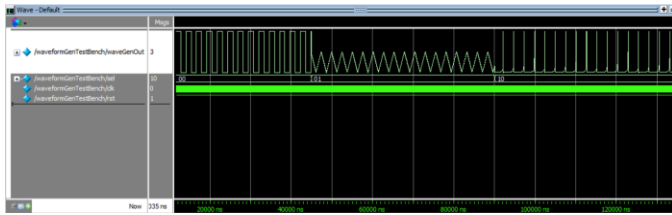


Fig. 9 Waveform generator output

2

| Flow Summary | |
|------------------------------------|---|
| Flow Status | Successful - Sat May 28 14:33:51 2022 |
| Quartus Prime Version | 20.1.0 Build 711 06/05/2020 SJ Lite Edition |
| Revision Name | WaveformGen |
| Top-level Entity Name | WaveformGen |
| Family | Cyclone IV E |
| Device | EP4CE6E22A7 |
| Timing Models | Final |
| Total logic elements | 107 / 6,272 (2 %) |
| Total registers | 8 |
| Total pins | 12 / 92 (13 %) |
| Total virtual pins | 0 |
| Total memory bits | 0 / 276,480 (0 %) |
| Embedded Multiplier 9-bit elements | 0 / 30 (0 %) |
| Total PLLs | 0 / 2 (0 %) |

Fig. 10 Synthesis summary

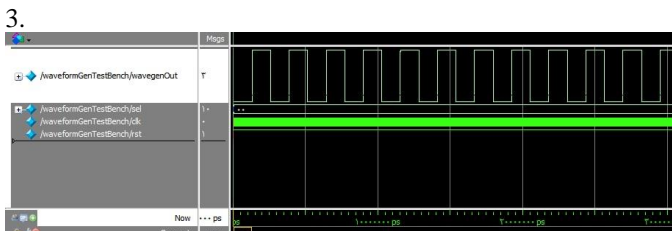


Fig. 11 Square waveform

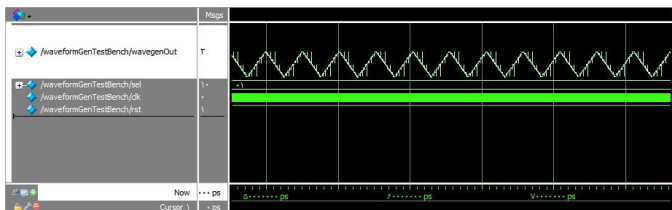


Fig. 12 Triangle waveform

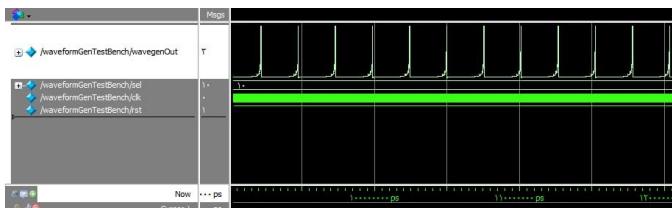


Fig. 13 Reciprocal waveform

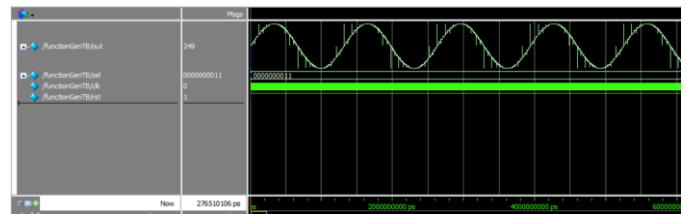


Fig. 14 Sin waveform

3.Frequency Selector

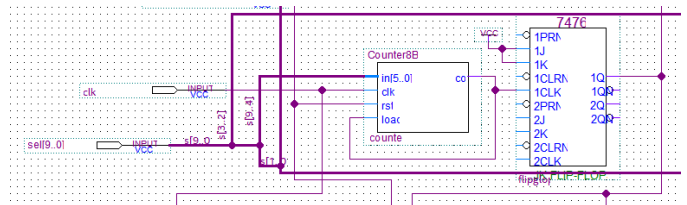


Fig. 15 Frequency Selector



Fig. 16 input = 9

The 8bit Counter loads 256 – input when Co(wired to load) becomes 1. 2 least significant bits of input are 2'b00 so input = {in, 2'b00}.

Output = $256 - \{9, 2'b00\} = 256 - 9 * 4 = 220$.

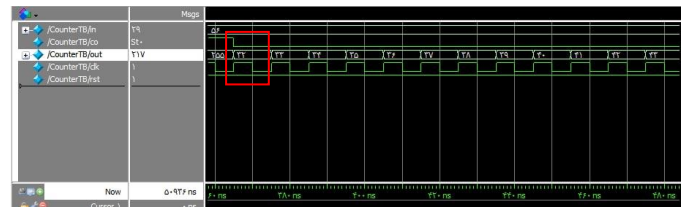


Fig. 17 input = 56

Output = $256 - \{56, 2'b00\} = 256 - 56 * 4 = 32$.

5.

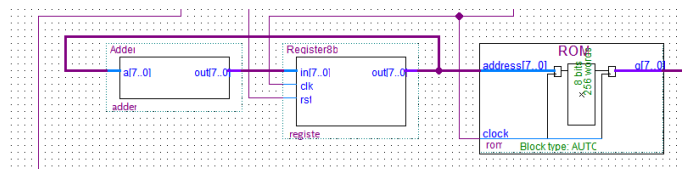


Fig. 18 DDS

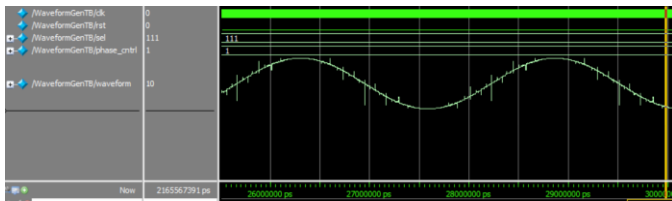


Fig. 19 Phase_ctrl = 1

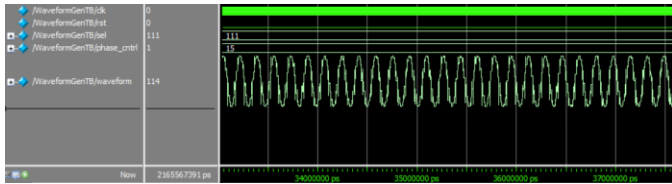


Fig. 19 Phase_ctrl = 15

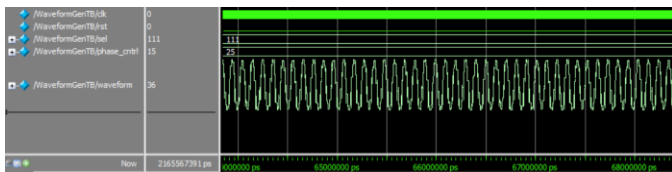


Fig. 20 Phase_ctrl = 25

When the value of Phase_ctrl is 1, every block of the rom will be shown but when the value of Phase_ctrl increases, some of the rom blocks will be skipped.

4. Amplitude Selector

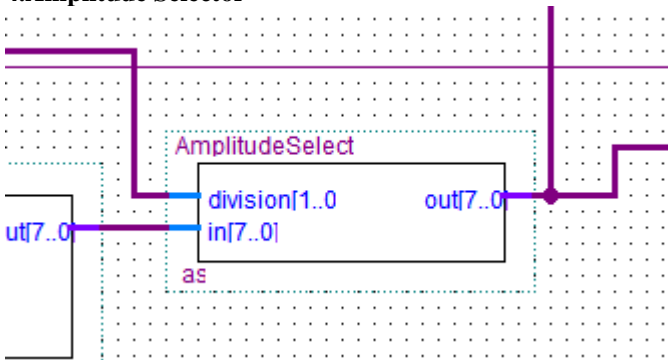


Fig. 21 amplitude selector

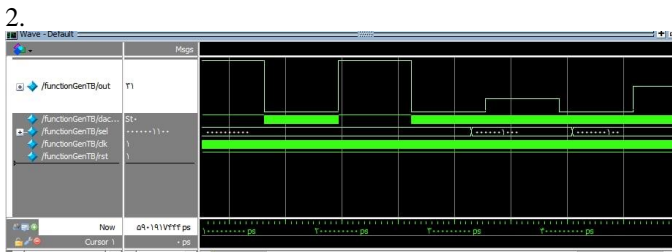


Fig. 22 Shifted Square

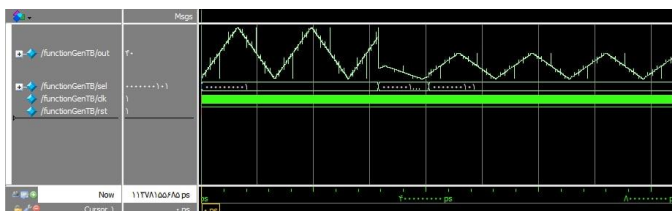


Fig. 23 Shifted Triangle

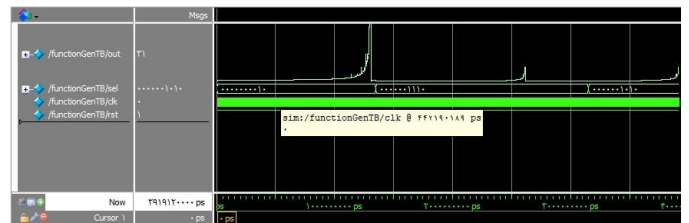


Fig. 24 Shifted Reciprocal

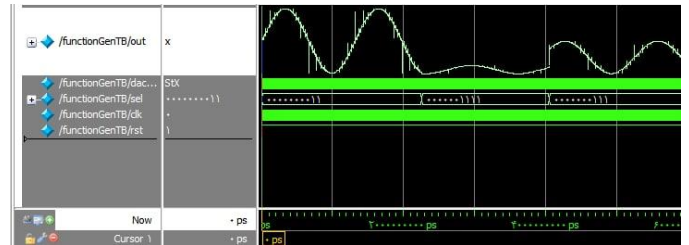


Fig. 25 Shifted Sin

5. The total design

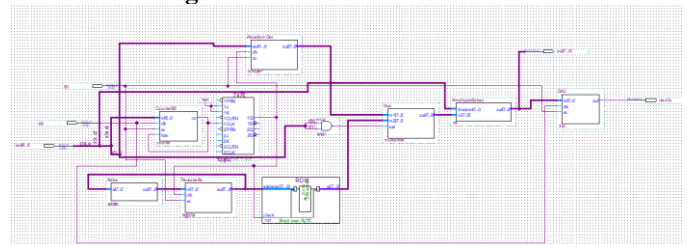


Fig. 26 Total design

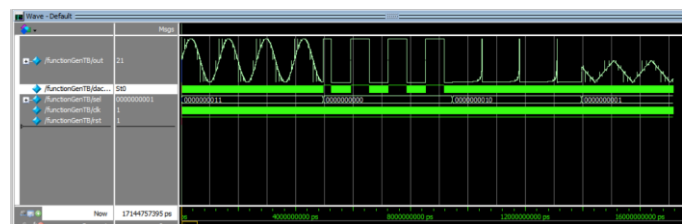


Fig. 27 Waveforms

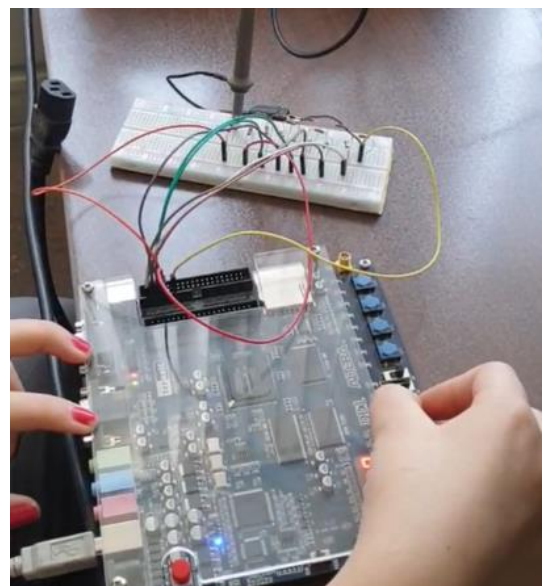


Fig. 28 Circuit

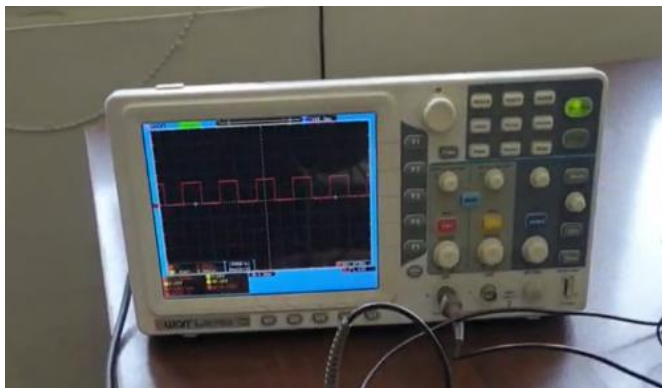


Fig. 29 Square Waveform without shift

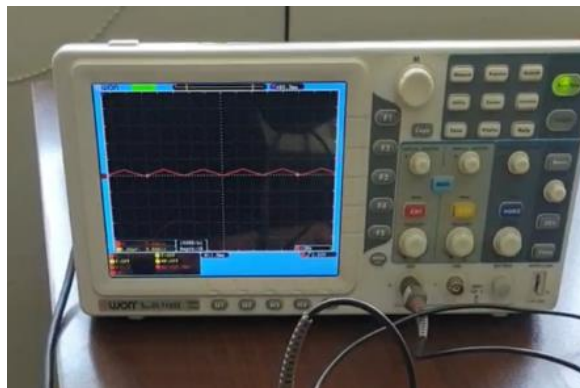


Fig. 33 Triangle Waveform with one shift

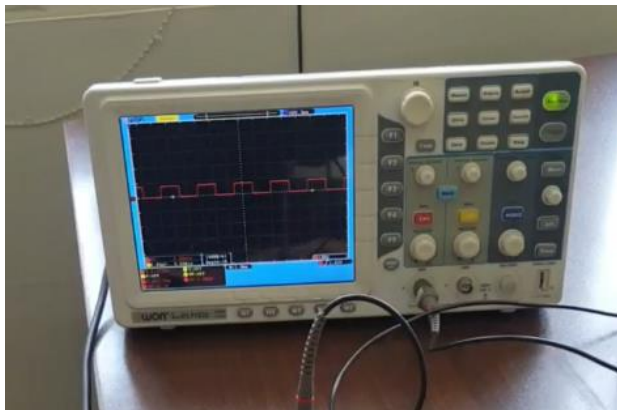


Fig. 30 Square Waveform with one shift

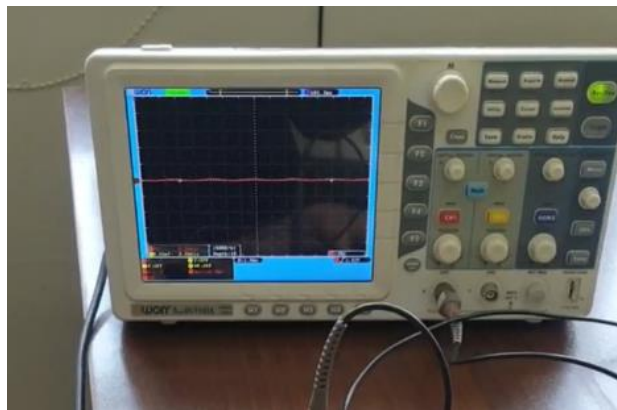


Fig. 34 Triangle Waveform with two shifts



Fig. 31 Square Waveform with two shifts

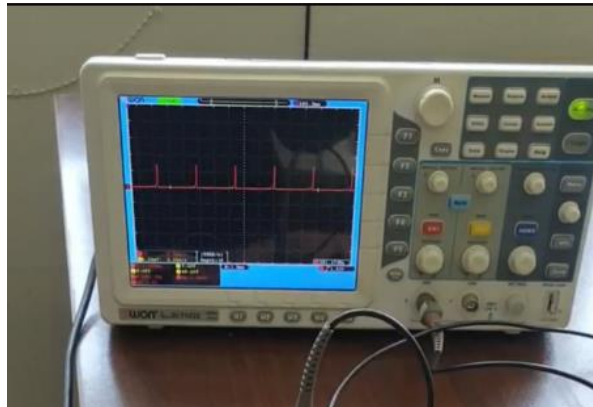


Fig. 35 Reciprocal Waveform without shift

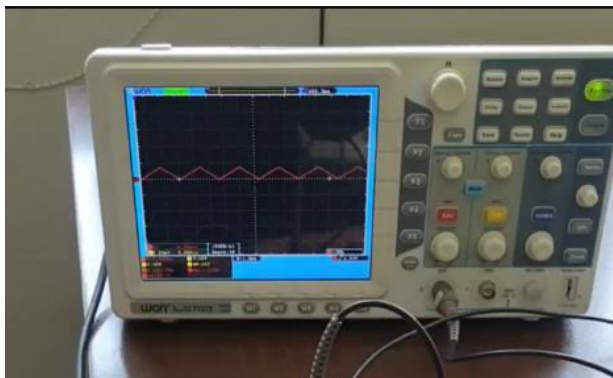


Fig. 32 Triangle Waveform without shift

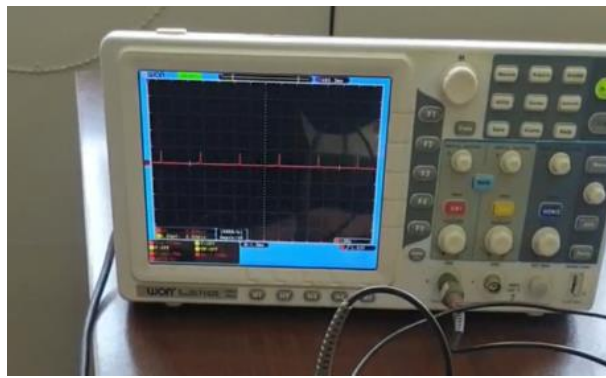


Fig. 36 Reciprocal Waveform with one shift

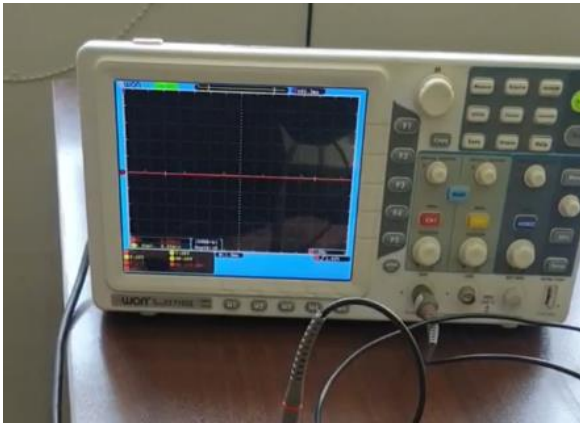


Fig. 37 Reciprocal Waveform with two shifts

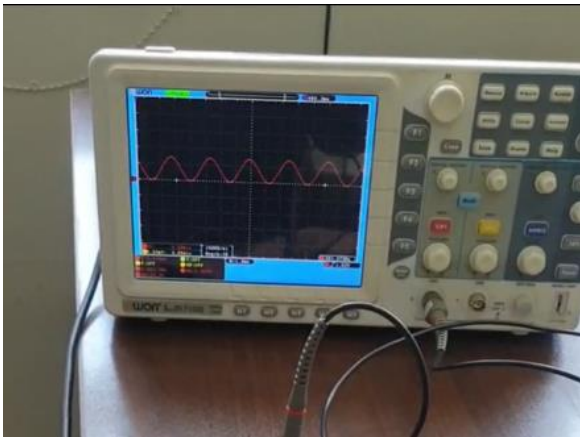


Fig. 38 Sin Waveform without shift

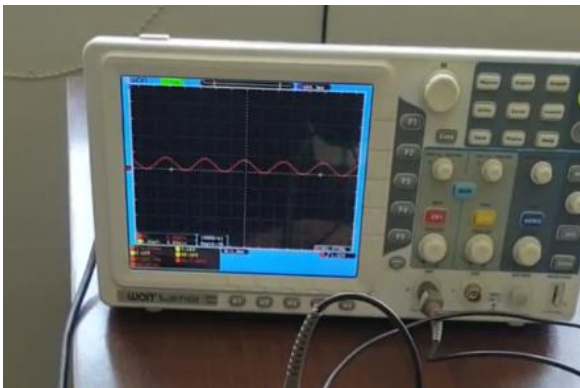


Fig. 39 Sin Waveform with one shift



Fig. 40 Sin Waveform with two shifts